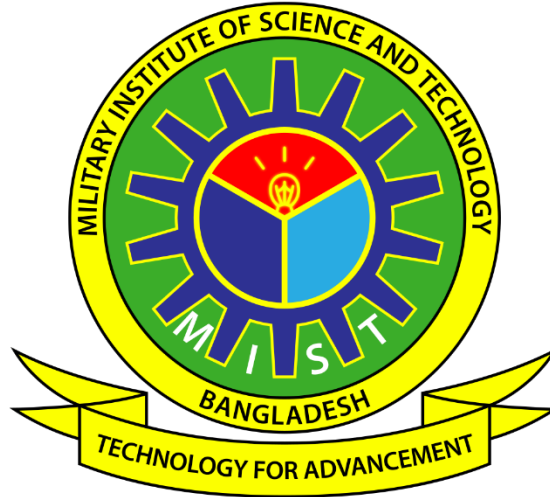


MILITARY INSTITUTE OF SCIENCE & TECHNOLOGY

Department of Electrical Electronic and Communication Engineering



Project name: The Electric Kaleidoscope.

Group no:08

Faculty members:

- Lt Col Md Aminul Islam
- Asst. Prof. A. A. M. Shah Sadman
- Lec Moumita Datta
- Lec Muhammed Zubair Rahman
- Lec Zia Md Galib Ul Alim

Group:08

Sec:A

Group Members	
Name	ID
Arshean Subah	202216011
Md. Sayeed Hasan	202216056
Md. Shahriar Abid Swapnil	202216058
Mahmud Hasan Asif	202216203
Dwip Das Joyonta	202116161
Kamruzzaman Pintu	202216023
Shabab Mahmud	202016082

Table of Contents

● Abstract.....	01
● Keywords	02
● Introduction.....	02
● Methodology.....	03
● Circuit diagram.....	06
● Procedure.....	07
● Simulation result.....	07
● Data table.....	09
● Calculation.....	09
● Error calculation.....	11
● Discussion.....	12
● Conclusion.....	13
● References.....	13



Abstract:

This groundbreaking project introduces a unified bridge circuit that integrates the fundamental principles of the Wheatstone bridge, Maxwell inductance bridge, and De Sauty capacitance bridge. By merging these established methodologies, this innovative design enables the simultaneous measurement of resistance, inductance, and capacitance in a single, streamlined configuration. The proposed combined bridge leverages the Wheatstone bridge's ability to accurately measure resistance, the Maxwell bridge's proficiency in determining inductance, and the De Sauty bridge's expertise in characterizing capacitance. Through a carefully orchestrated combination of these components, the circuit achieves a harmonious balance that allows for the precise determination of all three electrical parameters. This innovative approach offers significant advantages over traditional methods, which often require separate setups and measurements for each parameter. The combined bridge streamlines the measurement process, reduces errors associated with multiple setups, and enhances efficiency. Moreover, by providing a comprehensive understanding of a component's electrical properties, this integrated approach empowers engineers and researchers to optimize circuit design and performance. The project delves into the theoretical underpinnings of the combined bridge, exploring the mathematical relationships and balancing conditions that govern its operation. It also presents the experimental setup, including the selection of appropriate components, circuit configuration, and measurement techniques.

Keywords :

Combined bridge, Multi-parameter measurement, Resistance, Inductance, Capacitance, Wheatstone bridge, Maxwell inductance bridge, De Sauty capacitance bridge, Electrical component characterization, AC circuit, Balancing condition, Open-circuit technique, Simultaneous measurement, Circuit analysis, Electrical engineering, Electronics Circuit ,design Component ,testing Materials science, Innovation, Efficiency Accuracy, Precision, Measurement ,techniques, Electrical measurement, Instrumentation, Laboratory techniques.



Introduction:

The precise characterization of electrical components, including their resistance (R), inductance (L), and capacitance (C), is fundamental in various branches of electrical engineering. Traditionally, separate bridges like the Wheatstone bridge, Maxwell inductance bridge, and De Sauty capacitance bridge are employed to measure each parameter individually. This approach can be time-consuming, prone to errors due to multiple setups, and lacks a holistic understanding of a component's behavior.

This research project presents a novel design: a **combined multi-parameter bridge**. This innovative circuit merges the principles of the aforementioned bridges, enabling the **simultaneous measurement of resistance, inductance, and capacitance** in a single configuration. The bridge leverages the strengths of each individual bridge:

- **Wheatstone bridge:** Accurately determines resistance values.
- **Maxwell inductance bridge:** Measures inductance with high proficiency.
- **De Sauty capacitance bridge:** Characterizes capacitance effectively.

Our design incorporates **two fixed resistors, two variable resistors, two inductors, and two capacitors**. The key innovation lies in strategically connecting and selectively **open-circuiting** these elements depending on the parameter being measured. This allows the bridge to achieve a **balanced state** (zero current flow through the null detector) for each parameter, facilitating precise calculations. This unified approach offers significant advantages:

- **Enhanced Efficiency:** Simultaneous measurement reduces time and effort compared to sequential bridge setups.
- **Improved Accuracy:** Eliminates errors that could arise from repeated measurements and separate setups.
- **Comprehensive Characterization:** Provides a complete picture of a component's electrical behavior (resistance, inductance, and capacitance) through a single measurement.

Methodology:

A. Theoretical Discussion:

This combined multi parameter “Electric Kaleidoscope” measures the unknown resistance, inductance, capacitance after reaching the balanced state for each parameter.

The key components of a are:

- a) two fixed resistors
- b) two variable resistors
- c) two inductors

d) two capacitors

e) Ac source

f) Ammeter

Now, we will discuss the basics of each bridge circuits.

Wheatstone Bridge for Resistance measure:

The Wheatstone bridge is a simple electrical circuit used to measure an unknown resistance by balancing two legs of a bridge circuit. It consists of four resistors: R_1 , R_2 , R_3 , and R_x (the unknown resistance). R_1 and R_2 are known resistors, while R_3 is a variable resistor. A galvanometer is connected between the midpoints of the two legs.

When the bridge is balanced, the voltage drop across the galvanometer is zero. At this point, the ratio of the known resistors ($\frac{R_1}{R_2}$) is equal to the ratio of the unknown resistor and the variable resistor ($\frac{R_x}{R_3}$). Mathematically:

$$\frac{R_1}{R_2} = \frac{R_x}{R_3}$$

By rearranging the equation, we can solve for the unknown resistance:

$$R_x = \frac{R_1}{R_2} \times R_3$$

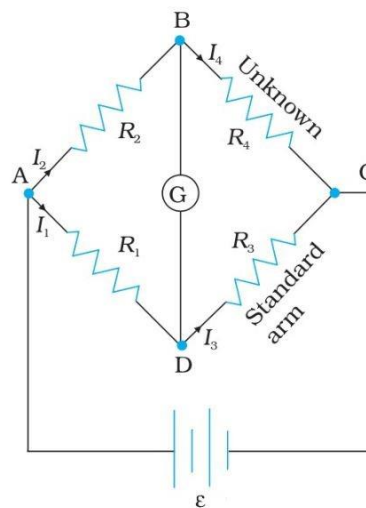


Fig 01: Wheatstone Bridge

MaxWell's Inductance Bridge for Inductance measure:

The Maxwell inductance bridge is a circuit used to measure unknown inductance. It consists of two inductors (L_1 and L_2), two resistors (R_1 and R_2), an AC source, and a null detector. When balanced, the following equation holds:

$$\frac{L_1}{L_2} = \frac{R_1}{R_2}$$

This allows for calculating L_2 using the known values of L_1 , R_1 , and R_2 . The bridge is simple but sensitive to frequency and component tolerances. It's used in various fields like electrical engineering and materials science.

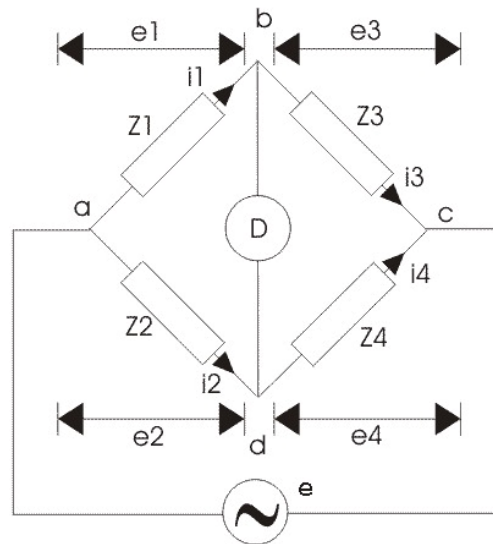


Fig02: MaxWell's Inductance Bridge.

De Sauty's Bridge for Capacitance measure:

The De-Sauty bridge is a simple AC circuit used to measure unknown capacitances. It consists of two known capacitors (C_1 and C_2), two resistors (R_3 and R_4), an AC source, and a null detector. When the bridge is balanced, the ratio of the known and unknown capacitances is equal to the ratio of the resistors. This allows for the calculation of the unknown capacitance. However, the bridge is limited to measuring lossless capacitors like air capacitors.

In De Sauty Bridge, the impedances of the arms are given by,

$$Z_1 = \frac{1}{j\omega C_1}$$

$$Z_2 = \frac{1}{j\omega C_2}$$

$$Z_3 = R_3$$

$$Z_4 = R_4$$

When the bridge is balanced, we get,

$$Z_1 \times Z_4 = Z_2 \times Z_3$$

$$\frac{1}{j\omega C_1} \times R_4 = \frac{1}{j\omega C_2} \times R_3$$

$$\frac{R_4}{C_1} = \frac{R_3}{C_2}$$

$$C_1 = \frac{R_4}{R_3} \times C_2$$

Here, C_1 is the unknown capacitor that we are measuring by using the bridge structure.

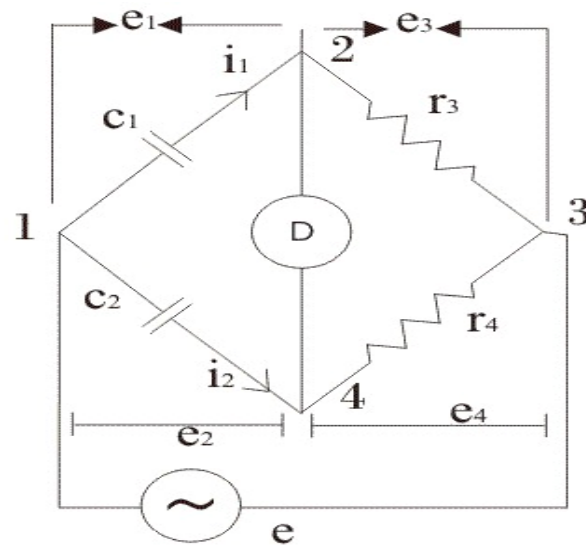


Fig03: De Sauty's Bridge.

The integration of various electrical components—specifically resistors, inductors, and capacitors—into a single circuit design offers significant advantages in measuring multiple parameters efficiently. This unified approach not only simplifies the instrumentation required but also enhances the precision of measurements through a balanced circuit configuration.

Circuit Design Overview

The design incorporates:

- **Two fixed resistors:** These provide a stable resistance value essential for maintaining consistent circuit behavior.
- **Two variable resistors:** These allow for adjustments in resistance, enabling calibration for different measurement scenarios.
- **Two inductors:** These components store energy in a magnetic field and help manage current flow, particularly in AC circuits.
- **Two capacitors:** These store energy electrostatically and can filter or smooth out voltage fluctuations.

Circuit diagram:

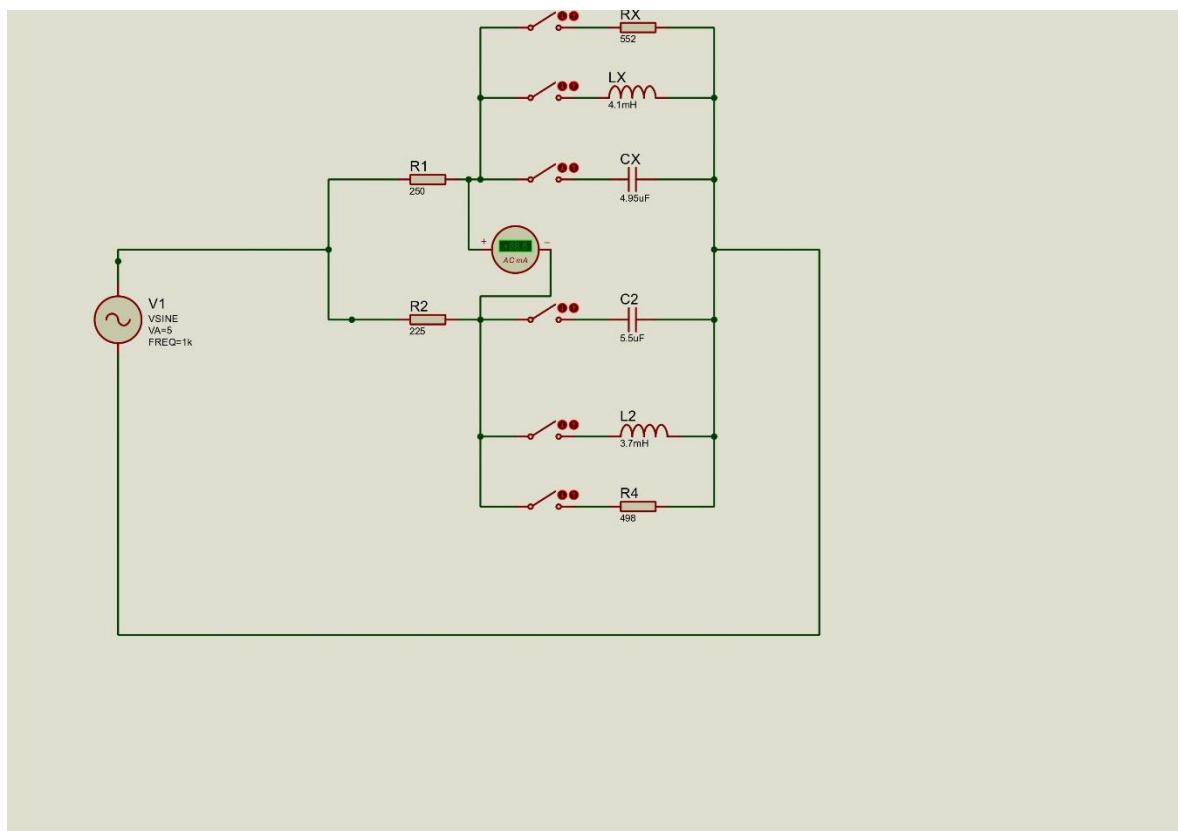



Fig04: General circuit

Procedure:

1. For resistor: the value of R_4 is chosen to be 498Ω .
2. For capacitor: the value of C_2 is chosen to be $2.8\mu\text{F}$.
3. For inductor: the value of L_2 is chosen to be 3.7mH .
4. Now, the value of R_x , C_x and L_x are determined from the experiment.


Simulation result:

For resistor:

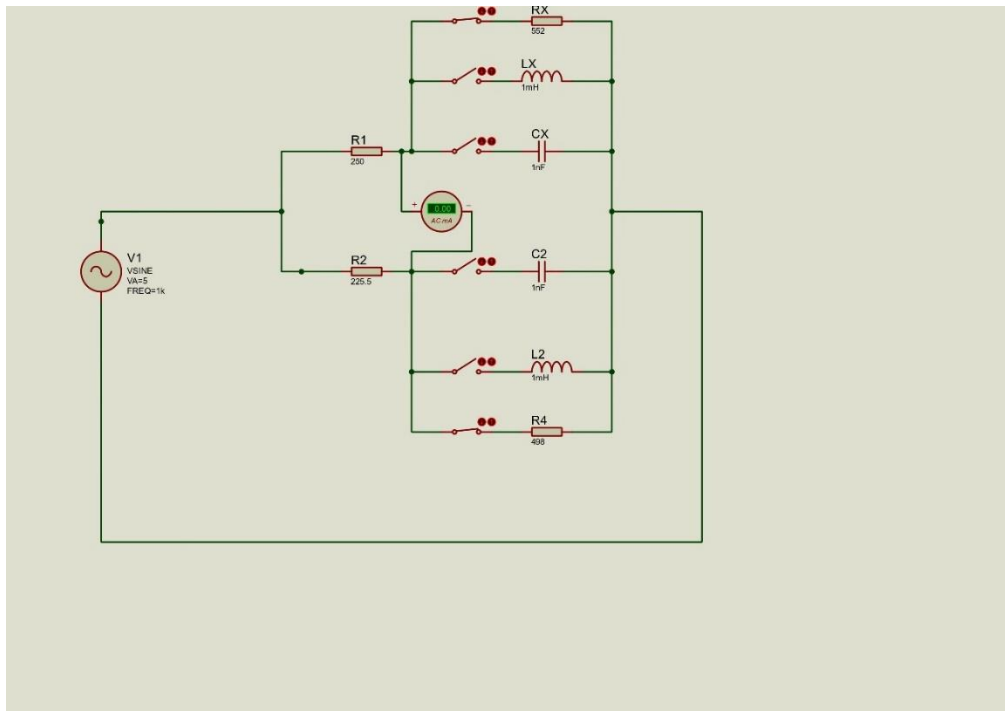


From the simulation diagram, we get the null deflection(0) using 552Ω resistor in R_x .

For capacitor:

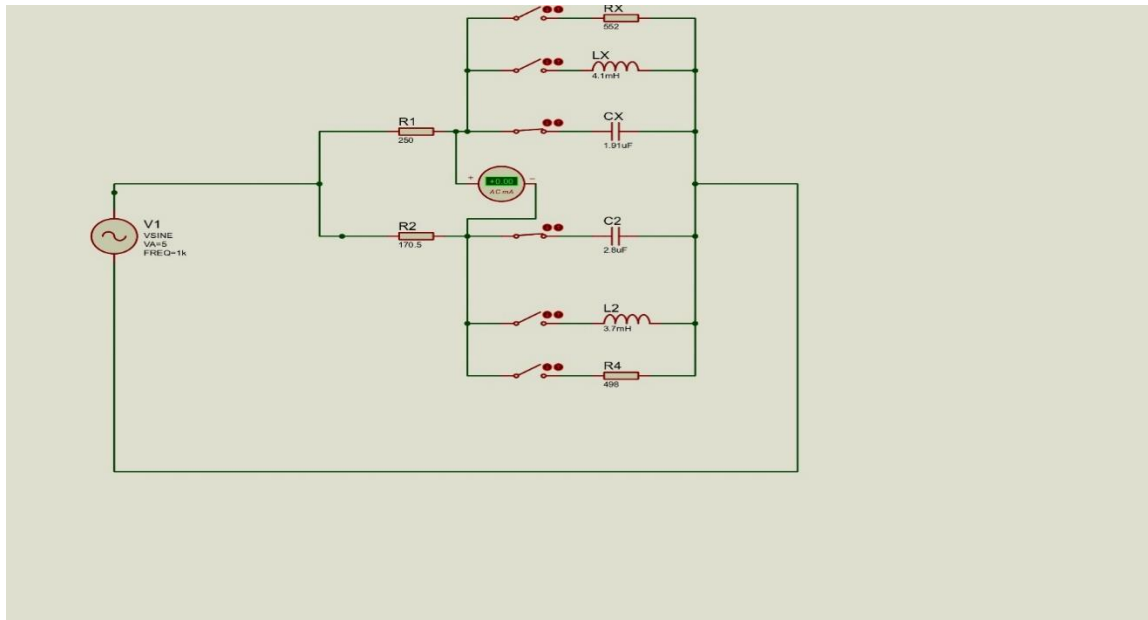

From the simulation diagram, we get the null deflection(0) using $1.91\mu\text{F}$ in C_x .

For inductor :

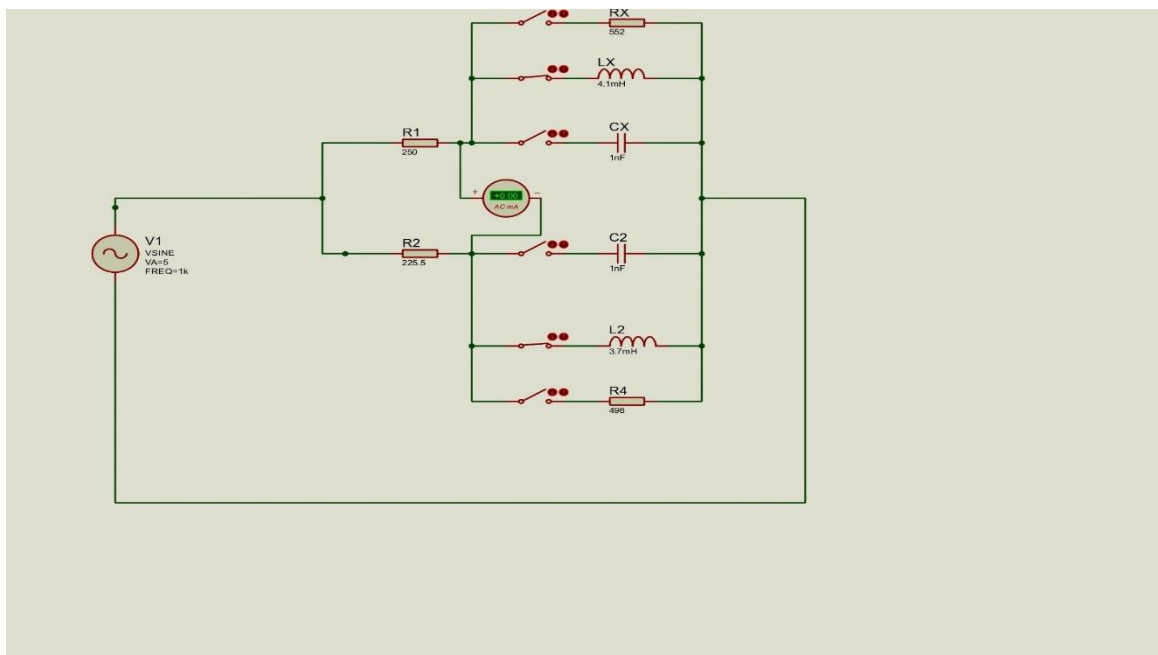

From the simulation diagram, we get the null deflection(0) using 4.7mH in L_x .

**Data Table:**

For resistor:

Serial No.	$V_{s(p)}$ (V)	R_1 Ω	R_2 Ω	R_4 Ω	R_X Measured	R_X Calculated	% Error
1.	5	250	170.5	498	730	730.205	0.028
2.	5	250	225.5	498	552	552.106	0.019

For capacitor:

Serial No.	$V_{s(p)}$ (V)	R_1 Ω	R_2 Ω	C_2 uF	C_X Measured	C_X Calculated	% Error
1.	5	250	170.5	2.8	1.91	1.9096	0.021
2.	5	250	225.5	5.5	4.95	4.961	0.22

For inductor:

Serial No.	$V_{s(p)}$ (V)	R_1 Ω	R_2 Ω	L_2 mH	L_X Measured	L_X Calculated	% Error
1.	5	250	170.5	2.4	3.52	3.519	0.028
2.	5	250	225.5	3.7	4.1	4.102	0.049



Calculation

Result:

For resistor:

$$R_X = \left(\frac{R_1}{R_2} \times R_4\right)\Omega$$

$$R_X = \left(\frac{250}{170.5} \times 498\right)\Omega$$

$$R_X = 730.20527\Omega.$$

For capacitor:

$$C_X = \left(\frac{R_1}{R_2} \times C_2\right)\mu F$$

$$C_X = \left(\frac{250}{170.5} \times 2.8\right)\mu F$$

$$C_X = 4.10557 \mu F.$$

For inductor:

$$L_X = \left(\frac{R_1}{R_2} \times L_2\right)mH$$

$$L_X = \left(\frac{250}{170.5} \times 2.4\right)mH$$

$$L_X = 3.51906 mH$$



Error calculation:

For resistor:

$$\begin{aligned}\text{Error} &= \frac{\text{Calculated} - \text{Measured}}{\text{Calculated}} \times 100 \% \\ &= \frac{730.205 - 730}{730.205} \times 100 \% \\ &= 0.028\%\end{aligned}$$

For capacitor:

$$\begin{aligned}\text{Error} &= \frac{\text{Calculated} - \text{Measured}}{\text{Calculated}} \times 100 \% \\ &= \frac{1.9096 - 1.91}{1.9096} \times 100 \% \\ &= 0.021\%\end{aligned}$$

For inductor:

$$\begin{aligned}\text{Error} &= \frac{\text{Calculated} - \text{Measured}}{\text{Calculated}} \times 100 \% \\ &= \frac{3.519 - 3.52}{3.519} \times 100 \% \\ &= 0.028\%\end{aligned}$$



Discussion:

The Electric Kaleidoscope experiment was a technical endeavor that showcased how merging traditional bridge circuits—Wheatstone, Maxwell, and De Sauty—can transform the way we approach electrical testing. This method not only enhances measurement accuracy but also offers significant advantages in efficiency and usability. Future modifications could further expand its functionality and applicability across various industries, solidifying its role as a versatile tool in both educational and professional settings. The potential for advancements in portability, digital integration, and sensitivity makes this device a promising candidate for ongoing research and development in electrical engineering.

Future Scops and Applications:

1. **Miniaturization:** Future developments could focus on miniaturizing the components to create a portable version of the Electric Kaleidoscope. This would enhance its usability in field applications where space and weight are critical.
2. **Digital Integration:** Incorporating digital displays or microcontroller interfaces could allow for real-time data logging and more sophisticated analysis of measurements. This integration could also facilitate automated calibration processes.
3. **Enhanced Sensitivity:** Modifications to improve the sensitivity of the circuit could be explored. This might involve using higher precision components or implementing advanced filtering techniques to reduce noise in measurements.
4. **Multi-Frequency Testing:** Expanding the design to support multi-frequency testing could enable more comprehensive analysis of components, particularly inductors and capacitors, which can behave differently at varying frequencies.
5. **Wireless Capability:** Implementing wireless communication features could allow remote monitoring and control of measurements, making it suitable for applications in IoT (Internet of Things) devices.
6. **Reduce complexity of measurement:** Electric Kaleidoscope eliminates the need for multiple setups, reducing the complexity involved in measuring resistance, inductance, and capacitance
7. **Saves Space:** The integration of three measurement functions into a single device significantly reduces the physical space required for instrumentation. This compact design is particularly advantageous in environments with limited workspace
8. **Reduces electricity consumption for measurement devices:** With fewer components drawing power simultaneously, the Electric Kaleidoscope not only becomes more energy-efficient but also contributes to a more sustainable approach to electrical testing.



Applications

- **Educational Tools:** It serves as an excellent educational instrument for teaching electrical engineering concepts, providing hands-on experience with circuit design and measurement techniques.
- **Quality Control in Manufacturing:** The device can be utilized in manufacturing processes to ensure that components meet specified resistance, inductance, and capacitance values before they are assembled **into larger systems**.
- **Research and Development:** In R&D environments, this multi-parameter measurement tool can facilitate the rapid characterization of new materials or components, speeding up innovation cycles.
- **Consumer Electronics Testing:** The Electric Kaleidoscope can be used to test consumer electronic devices for compliance with electrical standards, ensuring safety and performance.

Conclusion:

By combining traditional measurement techniques into a single circuit design, we not only improve efficiency and accuracy but also open doors to exciting future developments. As we look ahead, the potential for miniaturization, digital integration, and enhanced sensitivity promises to elevate this tool from a mere experiment to an essential instrument in both educational and professional realms.

References:

- [1] <https://www.elprocus.com/wheatstone-bridge-working-and-its-applications/>
- [2] <https://circuitglobe.com/maxwells-bridge.html>
- [3] <http://vlabs.iitkgp.ernet.in/asnm/exp11/index.html>
- [4] <https://www.eeeguide.com/maxwell-bridge-theory/>
- [5] <https://www.elprocus.com/what-is-maxwells-bridge-circuit-phasor-diagram-applications/>